

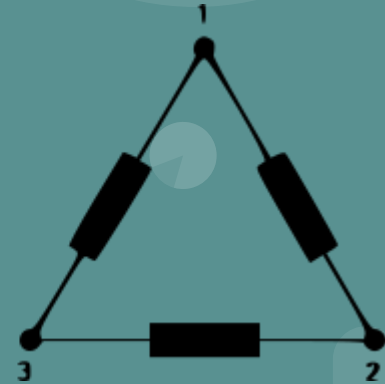


# Making Sense of Delta & Wye

By: Drew Matthews

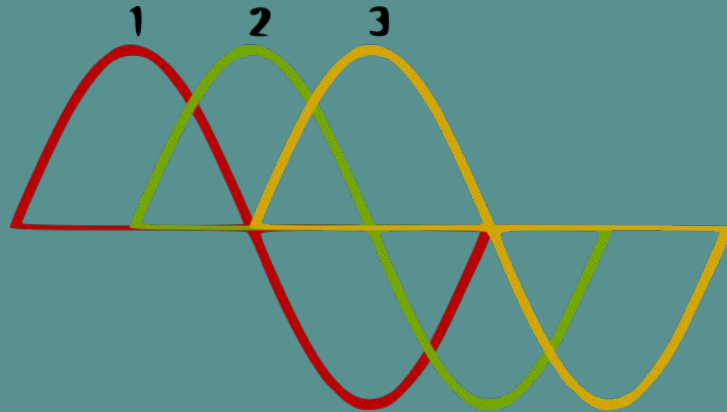


# Where Does Power Come From?

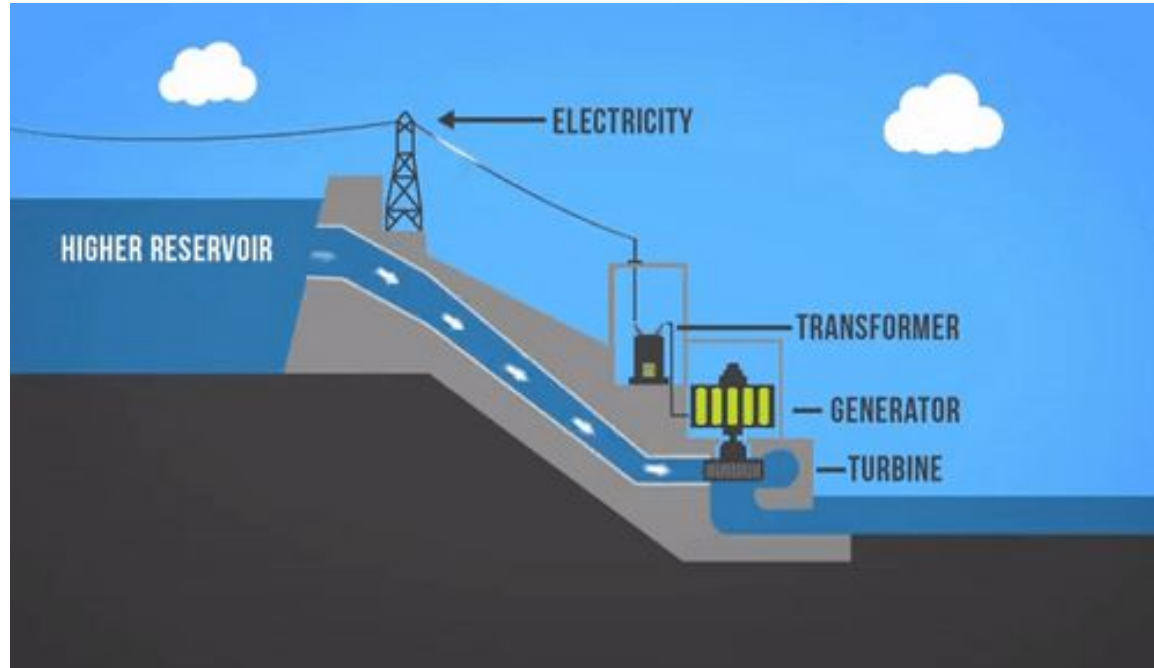




# How are the Three Phases Generated?

## The Generator

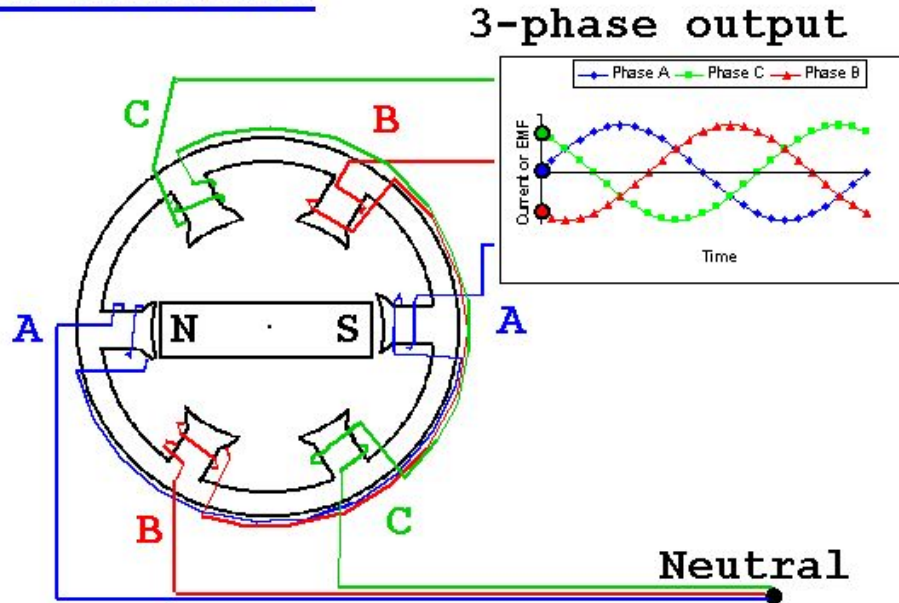




# Phase

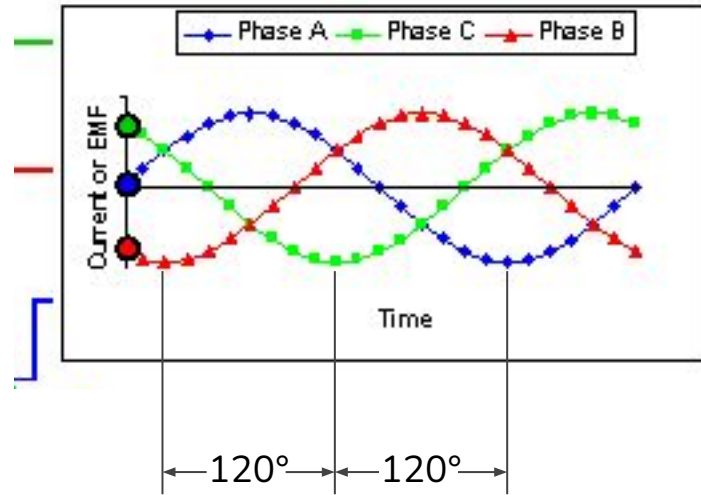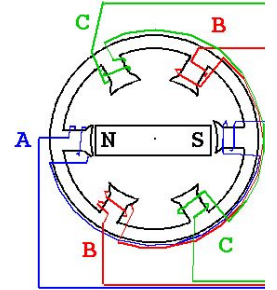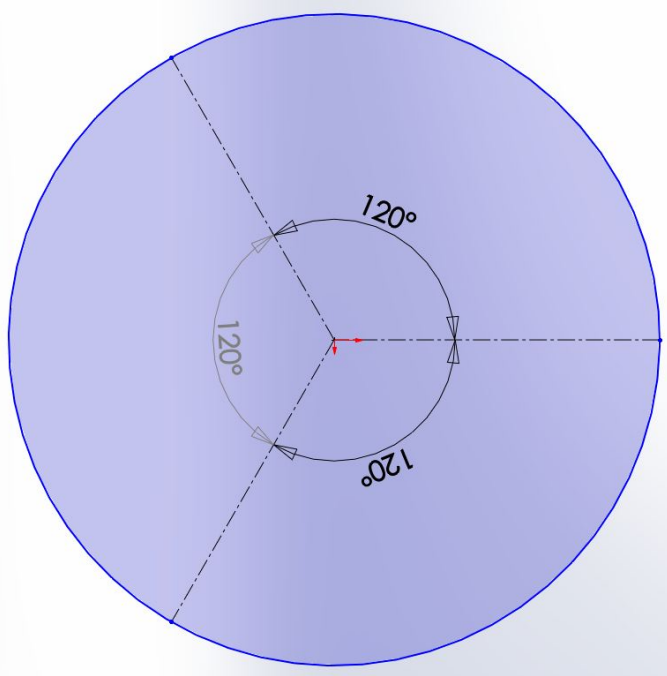

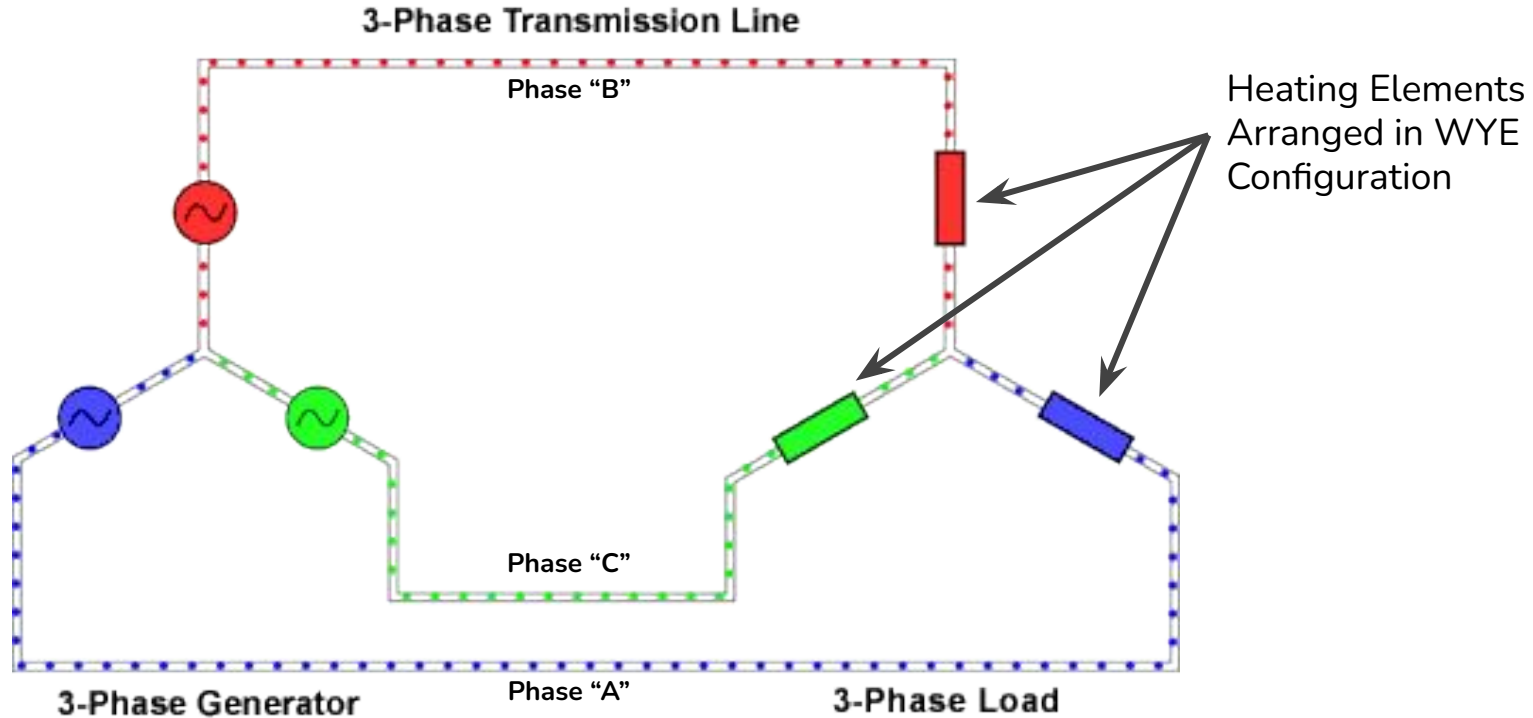
# Alternating Current (AC) Energy Flow

In North America  
the Energy Changes  
Directions 60 Times  
Per Second (60 Hz)

This is Why it is  
called "Alternating  
Current"



# How It's Transmitted

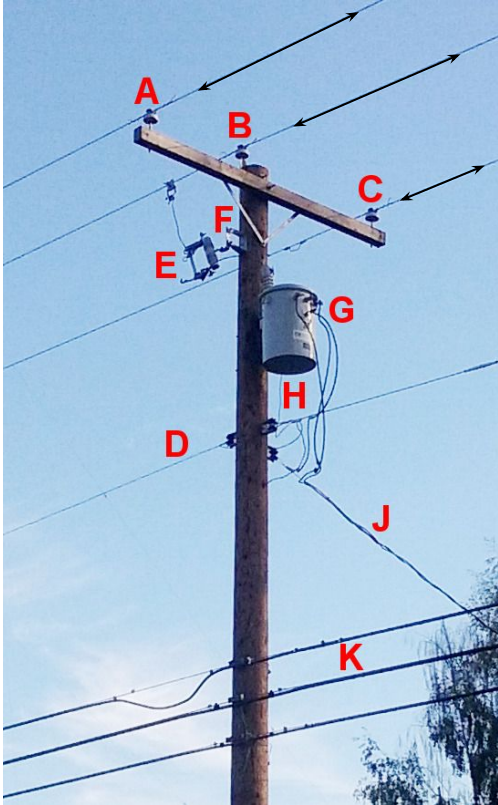

Typical North American utility pole, showing hardware for a residential 240/120 V split-phase [service drop](#):

(A,B,C) 3-phase primary distribution wires

(D) neutral wire

(E) fuse cutout

(F) lightning arrester

(G) single phase distribution transformer

(H) ground wire to transformer case

(J) "triplex" service drop cable carries secondary current to customer


(K) telephone and cable television cables



# Calculating the Difference
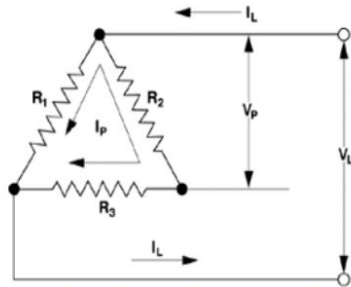
## 3-Phase Delta ( $\Delta$ )

A Delta configuration is a circuit in which three loads are connected in a "triangle" with each load representing a side of the triangle.




3-Phase Delta (Balanced Load)

$$\begin{aligned} I_p &= I_L / 1.73 \\ V_p &= V_L \\ W_{\text{DELTA}} &= 3(V_L^2) / R \\ W_{\text{DELTA}} &= 1.73 V_L I_L \end{aligned}$$

Figure 7 – 3-Phase Delta
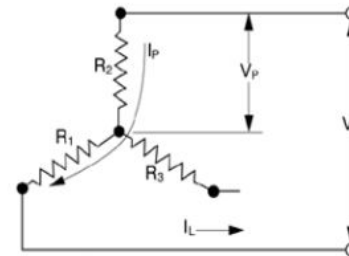
## 3-Phase Wye

A Wye configuration is a circuit in which three loads are connected in a Y with each load representing a leg of the Y. Figure 8 illustrates how a basic Wye circuit is laid out.



3-Phase Wye (Balanced Load)


$$\begin{aligned} I_p &= I_L \\ V_p &= V_L / 1.73 \\ W_{\text{WYE}} &= V_L^2 / R = 3(V_p^2) / R \\ W_{\text{WYE}} &= 1.73 V_L I_L \end{aligned}$$

WYE is typically used above 277VAC

Delta is typically used up to 277VAC

# How Output Changes “Broken Coil Delta” vs “Broken Line Delta”

## “Broken Coil DELTA” 3Ø Open Delta

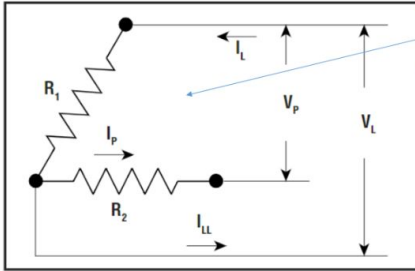

This Represents a Broken Coil which would be here.

$$V_P = V_L$$

$$W_T = 2V_L \times I_L$$

$$I_P = I_L$$

$$W_C = 2V_P \times I_P$$

$$V_L = V_P$$

$$W_T = 2(V_L^2 \div R_1)$$

$$I_L = I_P$$

$$I_{LL} = 1.73 \times I_P$$

$$2 \left( \frac{480^2}{38.4} \right) = 12000$$


Failure of an element in a three (3) element Delta circuit will reduce the wattage output by 33%

## “Broken Line DELTA”
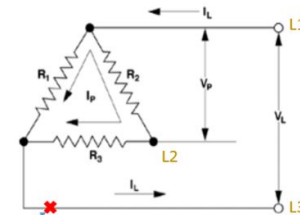
### 3-Phase Delta (Δ)

A Delta configuration is a circuit in which three loads are connected in a “triangle” with each load representing a side of the triangle.

Unbroken Heater Details:  
18kW Heater  
480V 3Phase  
With 3 - 6kW Coils  
21.65 Heater Amps  
21.65 Amps Per Leg  
38.4 Ω Per Coil (with no temp factor)  
25.6 Total Heater Ω



Broken Line

### 3-Phase Delta (Balanced Load)

$$I_P = I_L / 1.73$$

$$V_P = V_L$$

$$W_{DELTA} = 3(V_L^2) / R$$

$$W_{DELTA} = 1.73 V_L I_L$$

12.5 Amps through each coil when unbroken

From L1-L2:  
Resistance =  $R_2 = 38.4\Omega$   
Current = 12.5 Amps  
Wattage = 6000 Watts  
&  
Resistance =  $R_1 + R_3 = 76.8\Omega$   
Current = 6.25 Amps  
Wattage = 3000 Watts

Figure 7 – 3-Phase Delta

**Heater Output Watts:**  
6000+3000 = 9000 Watts

**Heater Output Watts:**  
12000 Watts




# How Output Changes “Broken Coil WYE” & “Broken Line WYE”

“Broken Line WYE”  
“Broken Coil WYE”

These are the same scenario  
on a 3-Wire WYE.

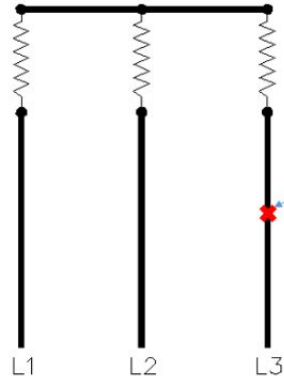Unbroken Heater Details:  
18kW Heater  
480V 3Phase  
With 3 - 6kW Coils  
21.65 Heater Amps  
21.65 Amps Per Leg  
12.79  $\Omega$  Per Coil (with no temp factor)  
25.6 Total Heater  $\Omega$



Broken Line

EACH COIL = 12.79  $\Omega$   
25.58  $\Omega$  FOR 2 IN SERIES  
480V / 25.58  $\Omega$  = 18.8 Amps  
18.8 A \* 480V = 9024 Watts

Heater Output Watts:  
9024 Watts



# Conclusion

Each Type Of Wiring Configuration (Delta And Wye) Have Their Own Unique Benefits. Now That We Know Their Differences We Can Use Their Benefits To Our Advantage In Order To Create An Optimal Heater Design.